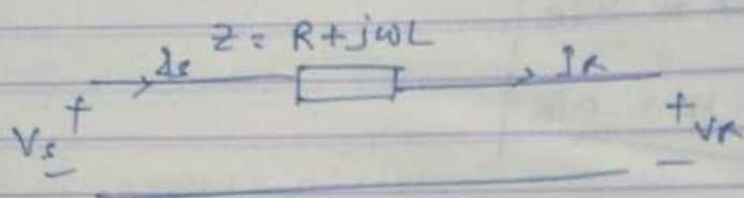


# ① ABCD parameters of Transmission Line

## (1) Short transmission Line -

In short transmission line only impedance is there



$$I_s = I_R = 0 \cdot V_R + 1 \cdot I_R$$

applying KVL in above loop we get.

$$V_s = V_R + I_R Z = 1 \cdot V_R + Z I_R$$


matrix form

\*\*

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

So, ABCD parameter is  $1, Z, 0, 1$

## (2) Admittance (Y) Network

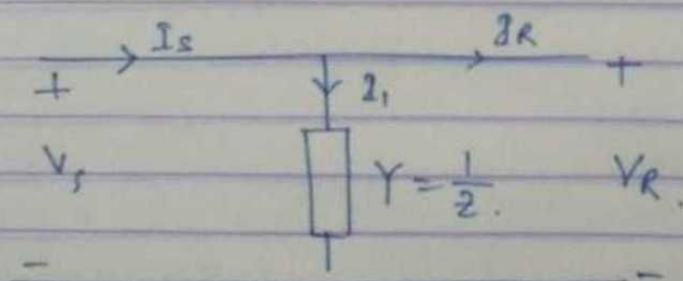

$$V_R = V_s = 1 \cdot V_R + 0 \cdot I_R$$

$$I_s = I_R + I_1$$

$$= I_R + V_R Y$$

$$= Y V_R + 1 \cdot I_R$$

$$\begin{aligned} I &= \frac{V}{Z} & Y &= \frac{1}{Z} \\ I &= \frac{V}{1/Y} \\ I &= V Y \end{aligned}$$


$$V_s = 1 \cdot V_R + 0 \cdot I_R$$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$


So, for the admittance network ABCD parameter is

$$\begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$

Admittance.

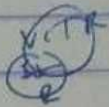


### (3) Cascading Networks

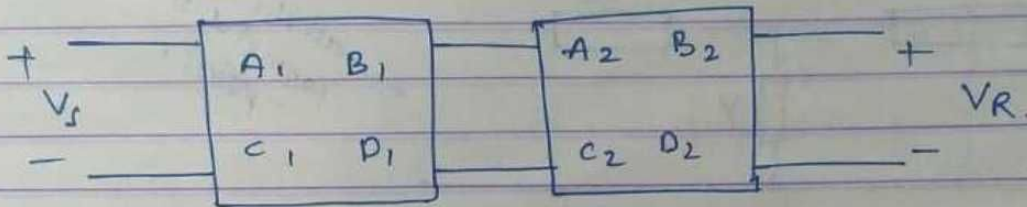

$$\begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \times \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} = \text{overall ABCD Parameter.}$$

### (4) Nominal T- Networks

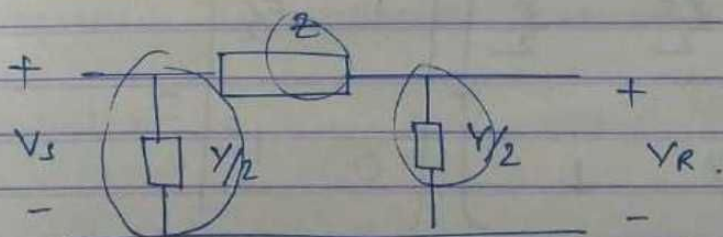

$$Y/2 \quad Z \quad Y/2$$


$$\begin{bmatrix} 1 & 0 \\ Y/2 & 1 \end{bmatrix} \times \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \times \begin{bmatrix} 1 & 0 \\ Y/2 & 1 \end{bmatrix} = \begin{bmatrix} 1 & Z \\ Y/2 & \frac{Y^2}{2} + 1 \end{bmatrix} \times \begin{bmatrix} 1 & 0 \\ Y/2 & 1 \end{bmatrix}$$



$$= \begin{bmatrix} 1 + \frac{Yz}{2} & z \\ \frac{Y}{2} + \frac{Y}{2} \left(1 + \frac{Yz}{2}\right) & 1 + \frac{Yz}{2} \end{bmatrix}$$

$$= \begin{bmatrix} 1 + \frac{Yz}{2} & z \\ Y \left(1 + \frac{Yz}{4}\right) & 1 + Yz \end{bmatrix}$$

6. Nominal T Network

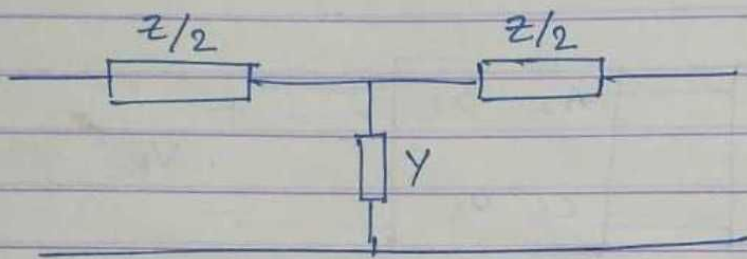

← all the capacitance is connected to the point.


$$\begin{bmatrix} 1 & z/2 \\ 0 & 1 \end{bmatrix} \times \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \times \begin{bmatrix} 1 & z/2 \\ 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 + \frac{Yz}{2} & \frac{z}{2} \\ Y & 1 \end{bmatrix} \begin{bmatrix} 1 & z/2 \\ 0 & 1 \end{bmatrix} =$$

$$\begin{bmatrix} 1 + \frac{Yz}{2} & \left(1 + \frac{Yz}{2}\right) \frac{z}{2} + \frac{z}{2} \\ Y & 1 + Yz/2 \end{bmatrix}$$

$$Z = \begin{bmatrix} 1 + \frac{Yz}{2} & z \left(1 + \frac{Yz}{4}\right) \\ Y & 1 + \frac{Yz}{2} \end{bmatrix}$$

⑥ End condenser Network

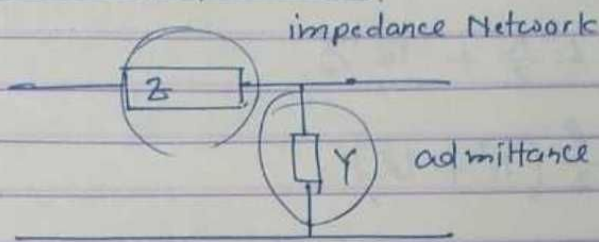


$$\begin{bmatrix} 1 & z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} = \begin{bmatrix} 1 + Yz & z \\ Y & 1 \end{bmatrix}$$

$A \neq D$ , so, this network is not symmetrical.


$$AD - BC = 1 \rightarrow \text{Reciprocal.}$$

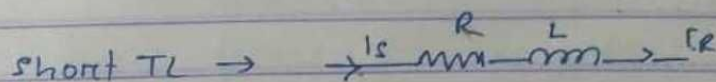$\Rightarrow$  power losses in Transmission line  $\rightarrow$



$$P_{Loss} = I_s^2 R = I_R^2 R.$$


Nominal  $\Pi$ -Network  $\rightarrow$

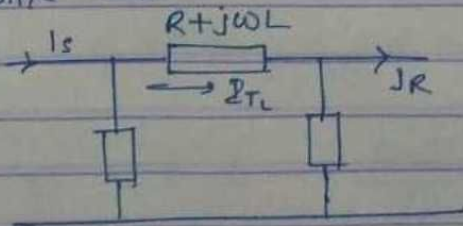

$$P_L = I_{TL}^2 R.$$



## Nominal T Network -

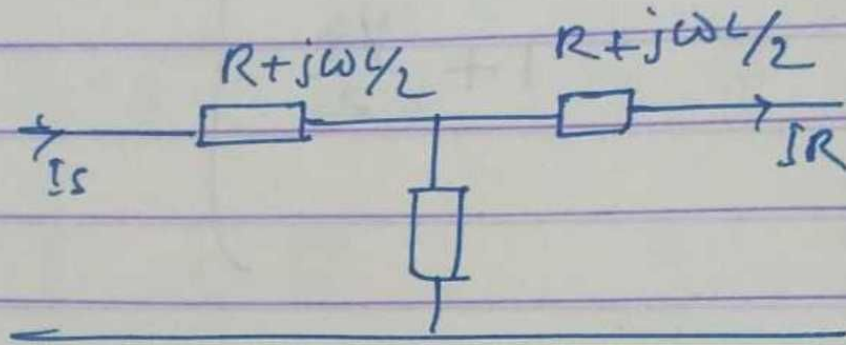

power loss.

$$P_L = I_s^2 \frac{R}{2} + I_R^2 \frac{R}{2}$$

$$= \frac{R}{2} (I_s^2 + I_R^2)$$