

- Principles of Teleommunication
- Module 2\_Amplitude Modulation
- Lecture Plan \_ Part4

## 1. Generation of AM Waves


The circuit that generates the AM waves is called as amplitude modulator and in this post we will discuss two such modulator circuits namely :

(a) Square Law Modulator

(b) Switching Modulator
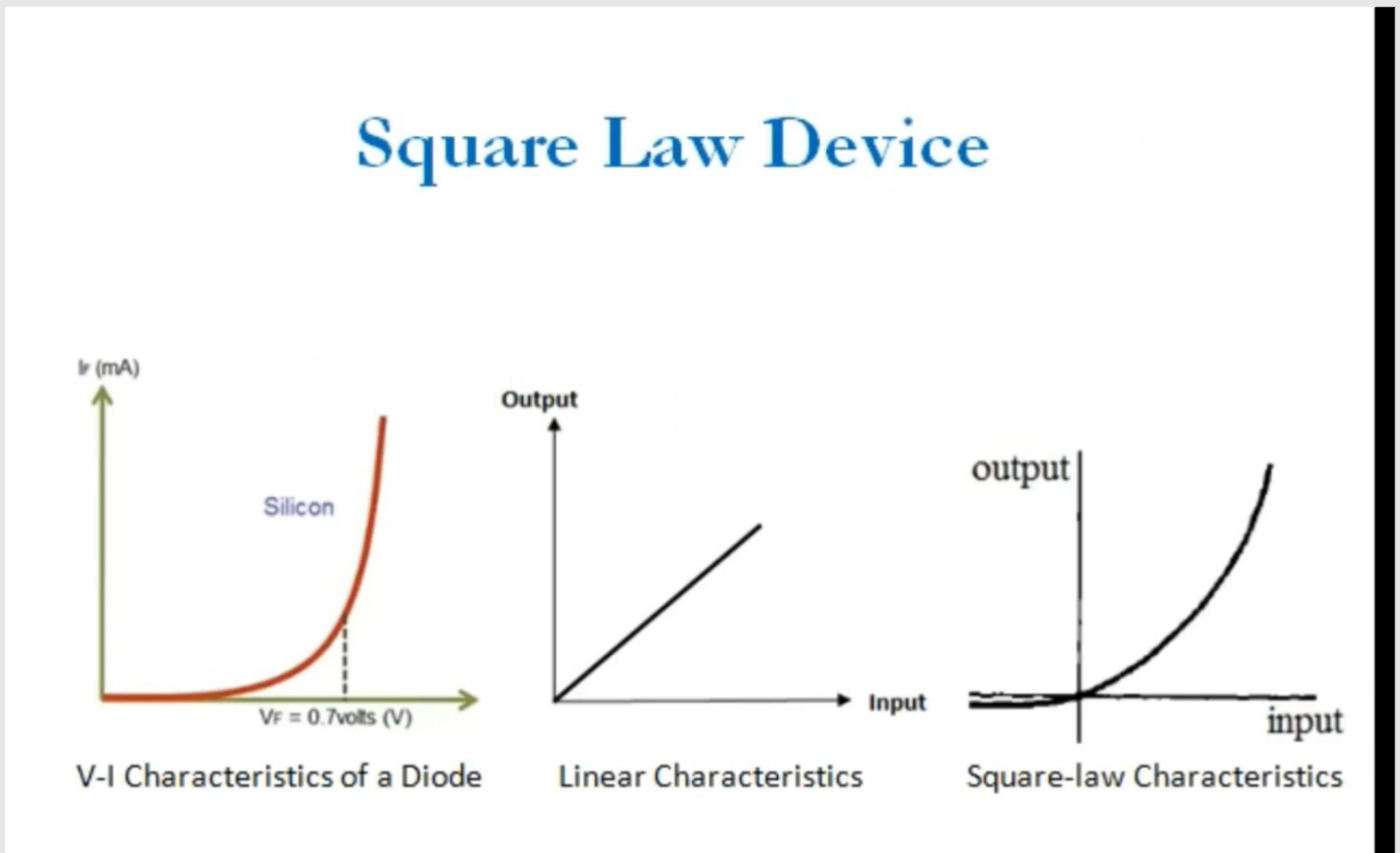
# Square law device

- Both the above circuit use a non linear element such as diode for their implementation.



Diode



Non-linear device



Used in those circuits



Linear



Non-linear


relation

between its

current &  
voltage

( diode )


## (a) Square Law Modulator

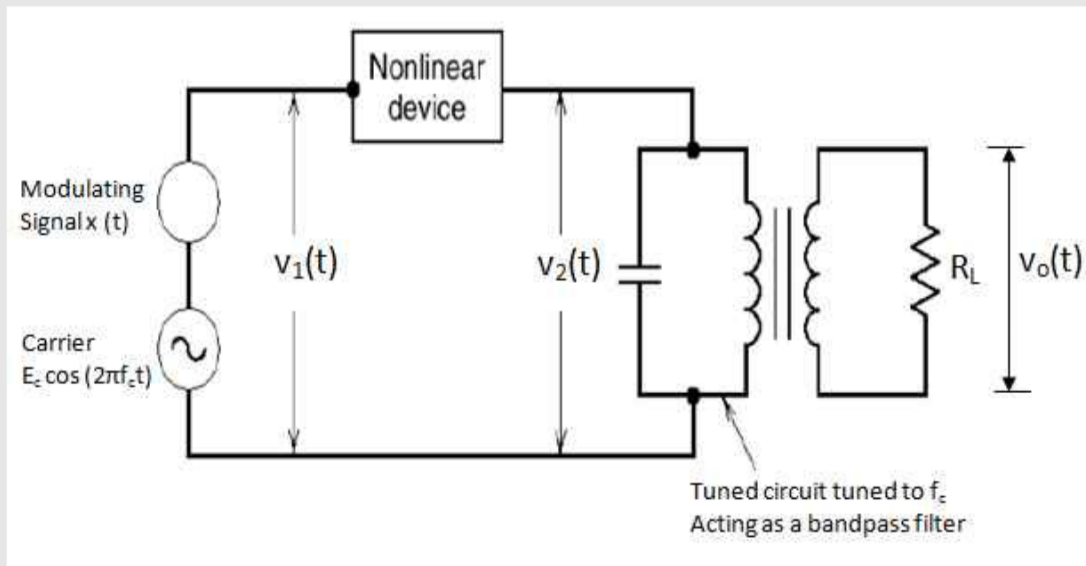

Square law modulator consist of -

- A non-linear device
- A bandpass filter
- A carrier source and modulating signal

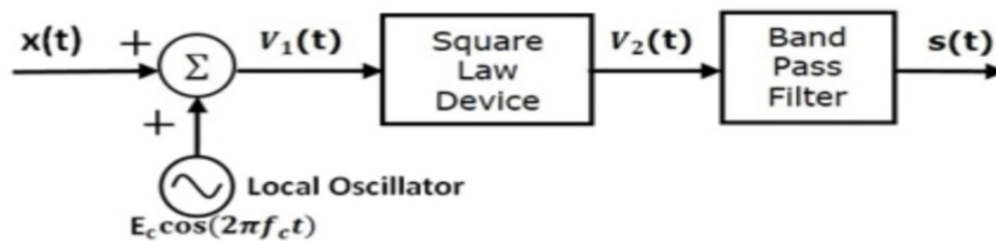The modulating signal and carrier are connected in series with each other and their sum  $v_1(t)$  is applied at the input of the non-linear device, such as diodes and transistor.



$$v_1(t) = x(t) + c(t)$$

$$v_1(t) = x(t) + E_c \cos(2\pi f_c t) \quad \dots\dots\dots(1)$$

The input output relation for square law device is given as:

$$v_2(t) = av_1(t) + bv_1^2(t) \quad \dots\dots\dots(2)$$

Where a and b are constants

Now substituting expression (1) in (2), we get


$$v_2(t) = a[x(t) + E_c \cos(2\pi f_c t)] + b[x(t) + E_c \cos(2\pi f_c t)]^2$$

Or,

$$v_2(t) = ax(t) + aE_c \cos(2\pi f_c t) + b[x^2(t) + 2x(t) \cos(2\pi f_c t) + E_c^2 \cos^2(2\pi f_c t)]$$

Or,
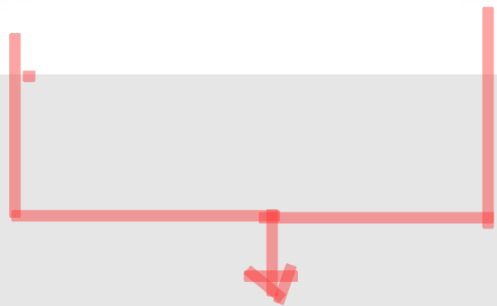
$$v_2(t) = \underbrace{ax(t)}_{(1)} + \underbrace{aE_c \cos(2\pi f_c t)}_{(2)} + \underbrace{bx^2(t)}_{(3)} + \underbrace{2bx(t) \cos(2\pi f_c t)}_{(4)} + \underbrace{bE_c^2 \cos^2(2\pi f_c t)}_{(5)}$$



Useful terms (2 & 4)

The five terms in the expression for  $v^2(t)$  are as under :

- Term 1:  $a x(t)$  : Modulating Signal
- Term 2 :  $a E_c \cos (2\pi f_c t )$  : Carrier Signal
- Term 3 :  $b x^2 (t)$  : Squared modulating Signal
- Term 4 :  $2 b x(t) \cos ( 2\pi f_c t )$  : AM wave with only sidebands
- Term 5 :  $b E_c^2 \cos^2 (2\pi f_c t )$  : Squared Carrier


**Out of these five terms, terms 2 and 4 are useful whereas the remaining terms are not useful.**

Next the LC tuned filter acts as a bandpass filter. It is tuned to frequency  $f_c$  and its bandwidth is equal to  $2f_m$ .

This bandpass filter eliminates the unuseful terms from the equation of  $v^2 (t)$ .

Figure:

Response of  
Band pass  
filter -

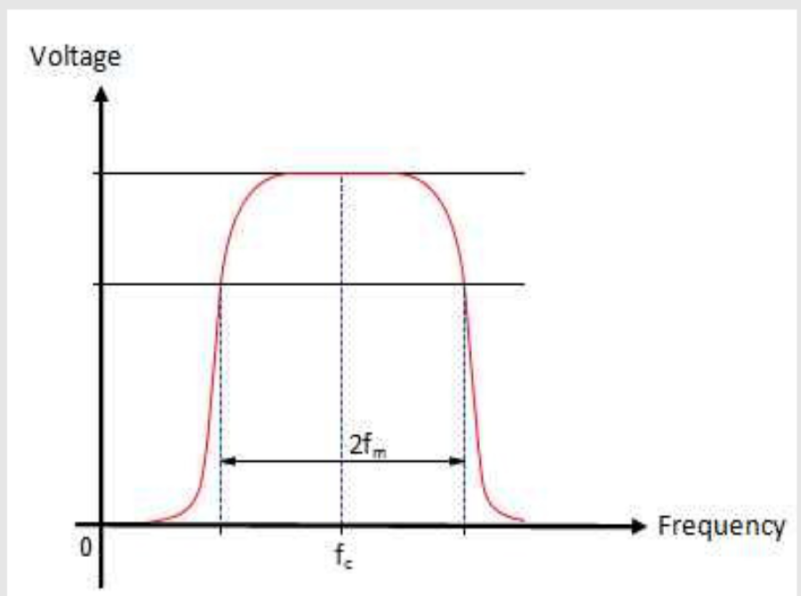

Output of the BPF can be written as:

$$V_o(t) = aE_c \cos(2\pi f_c t) + 2bx(t)E_c \cos(2\pi f_c t)$$

Or,

$$V_o(t) = [aE_c + 2bx(t)E_c] \cos(2\pi f_c t)$$

Or,

$$V_o(t) = aE_c \left[ 1 + \frac{2b}{a} x(t) \right] \cos(2\pi f_c t) \dots\dots\dots(3)$$

Comparing this with the expression for standard AM wave. i.e.;

$$s(t) = E_c [1 + mx(t)] \cos(2\pi f_c t)$$

We find that the expression for  $V_o(t)$  of equation (3) represents an AM wave with  $m = (2b/a)$ .


Hence, square law modulator produces  
an AM wave.

## (b) Switching Modulator


- The switching modulator using a diode has been shown in figure below.
- This diode is assumed to be operating as a switch .
- The modulating signal and carrier signal are connected in series with each other.
- The input voltage to the diode is given by :

$$V_1(t) = e(t) + x(t) = E_c \cos(2\pi f_c t) + x(t)$$

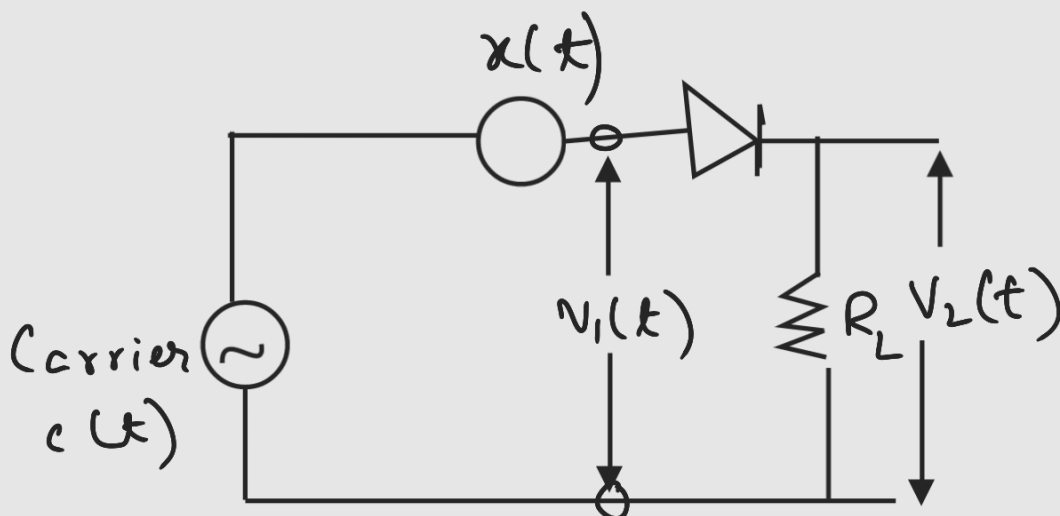- The amplitude of carrier is much larger than that of  $x(t)$  and  $c(t)$  decides the status of the diode (ON or OFF) .



a) Switching modulator

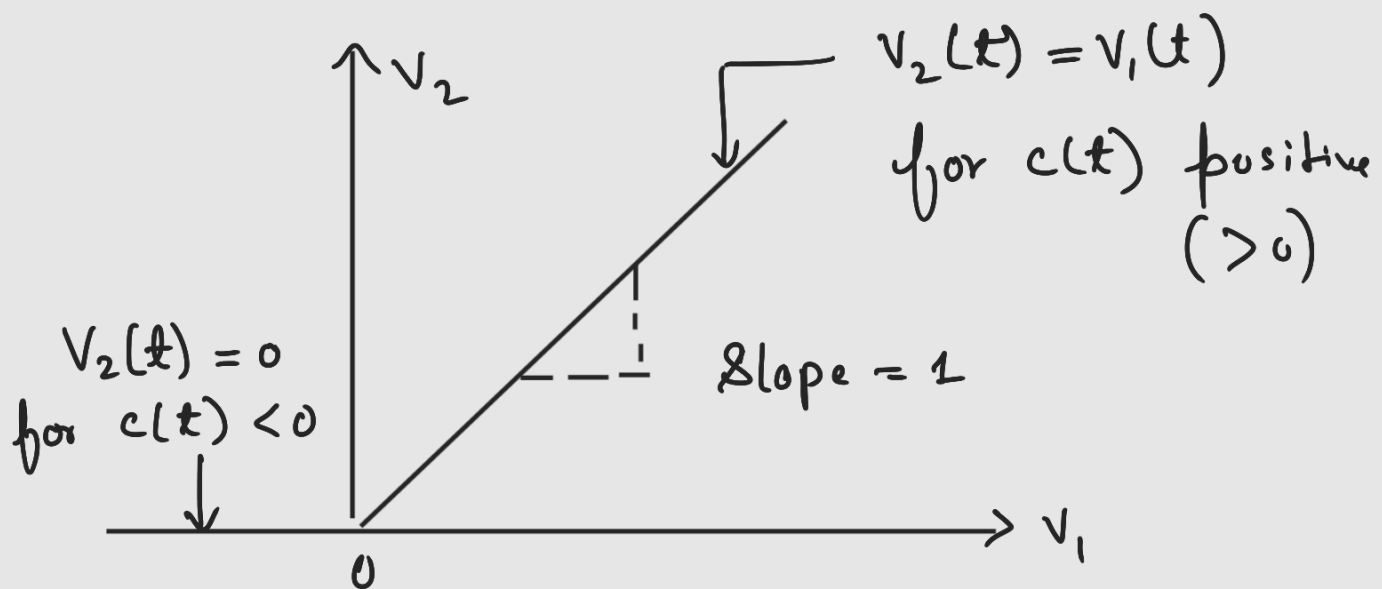

b) Idealized input-output relation

## Working Operation and Analysis

Let us assume that the diode acts as an ideal switch .

- **Closed switch- forward biased** in the positive half cycle of the carrier and offers zero impedance .
- **Open switch - reverse biased** in the negative half cycle of the carrier and offers an infinite impedance .
- Therefore, the output voltage

$v_2(t) = v_1(t)$  in the positive half cycle of  $c(t)$

$v_2(t) = 0$  in the negative half cycle of  $c(t)$  .



We can express  $v_2(t)$  mathematically as under :

$$v_2(t) = v_1(t) \cdot g_p(t) = [x(t) + E_c \cos(2\pi f_c t)] g_p(t)$$

.....(4)

where,  $g_p(t)$  is a periodic pulse train of duty cycle equal to one half cycle period i.e.  $T_0 / 2$  (where  $T_0 = 1/f_c$ ) .

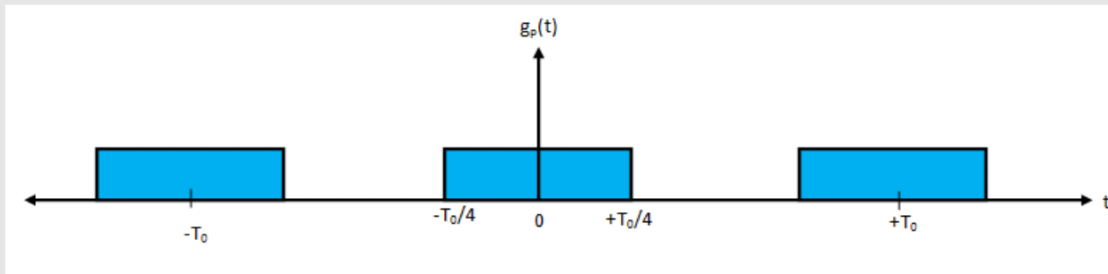


Fig.4

Let us express  $g_p(t)$  with the help of Fourier series as under :

$$g_p(t) = \frac{1}{2} + \frac{2}{\pi} \sum_{n=1}^{\infty} \frac{(-1)^{n-1}}{2n-1} \cos [2\pi f_c t(2n-1)]$$

.....(5)

$$g_p(t) = \frac{1}{2} + \frac{2}{\pi} \cos(2\pi f_c t) + \text{odd harmonic components}$$

.....(6)

Substituting  $g_p(t)$  into equation (4), we get

$$v_2(t) = [x(t) + E_c \cos(2\pi f_c t)] \left\{ \frac{1}{2} + \frac{2}{\pi} \sum_{n=1}^{\infty} \frac{(-1)^{n-1}}{2n-1} \cos[2\pi f_c t(2n-1)] \right\}$$

Therefore,

$$v_2(t) = [x(t) + E_c \cos(2\pi f_c t)] \left\{ \frac{1}{2} + \frac{2}{\pi} \cos(2\pi f_c t) + \text{odd harmonics} \right\}$$

.....(7)

The odd harmonics in this expression are unwanted, and therefore, are assumed to be eliminated .

Hence,

$$v_2(t) = \underbrace{\frac{1}{2}x(t)}_{\text{Modulating Signal}} + \underbrace{\frac{1}{2}E_c \cos(2\pi f_c t) + \frac{2}{\pi}x(t) \cos(2\pi f_c t)}_{\text{AM Wave}} + \underbrace{\frac{2E_c}{\pi} \cos^2(2\pi f_c t)}_{\text{Second harmonic of carrier}}$$

In this expression, the first and the fourth terms are unwanted terms whereas the second and third terms together represents the AM wave .

Clubbing the second and third terms together , we obtain

$$v_2(t) = \frac{E_c}{2} \left[ 1 + \frac{4}{\pi E_c} x(t) \right] \cos(2\pi f_c t) + \text{unwanted terms}$$

This is the required expression for the AM wave with  $m = [4/\pi E_c]$ . The unwanted terms can be eliminated using a band-pass filter (BPF) .

